

# **Endüstriyel Otomatik Kontrol Sistemleri**

**Y.Doç.Dr. Tuncay UZUN, EHM 014 6105 1 Ekim 2009**

**Dersin Konusu: Endüstriyel Otomatik Kontrol Sistemlerinde Kullanılan Algılayıcılar, Dönüştürücüler ve Uygulamaları**

## **Dersin Amacı:**

**Endüstriyel otomatik kontrol sistemlerinde kullanılan algılayıcılar ve dönüştürücülerin özellikleri, iç donanımı ve elektronik devrelerinin incelenmesi, uygulama devrelerinin analizi, incelenmesi ve tasarlanmasının öğretilmesidir.**

**Proje Teslim Tarihi: 15 Ekim 2009**

## **2.Endüstriyel Otomatik Kontrol Sistemlerinde Kullanılan Algılayıcılar (sensors), Dönüştürücüler (transducers) ve Uygulamaları**

### **2.1. Algılayıcı seçiminde kullanılan ölçütler**

**2.1.1. Duyarlılık**

**2.1.2. Doğrusallık**

**2.1.3. Sınırlar**

**2.1.4. Yanıt süresi**

**2.1.5. Doğruluk**

**2.1.6. Tekrarlanabilirlik**

**2.1.7. Ayırıcılık**

**2.1.8. Çıkışın tipi**

### **2.2. Dönüştürücülerin fiziksel karakteristikleri**

**2.2.1. Büyüklük ve ağırlık**

**2.2.2. Güvenirlik**

**2.2.3. Arabirim**

### **2.3. Dönüştürücülerin gruplanması**

**2.3.1.1. Aktif/Pasif dönüştürücüler**

**2.3.1.2. Temaslı/Temassız dönüştürücüler**

## **2.3.2. Temaslı dönüştürücüler**

### **2.3.2.1. Anahtarlar**

### **2.3.2.2. Piezoelektrik dönüştürücüler**

### **2.3.2.3. Konum ve yer değiştirmeyi algılama**

#### **2.3.2.3.1. Potansiyometreler**

##### **2.3.2.3.1.1. Doğrusal hareketli (Lineer, sürgülü)**

##### **2.3.2.3.1.2. Dairesel hareketli (Rotary pot.)**

#### **2.3.2.3.2. Doğrusal değişen farksal transformatör (LVDT)**

#### **2.3.2.3.3. Mutlak optik kodlayıcı**

#### **2.3.2.3.4. Artırmalı optik kodlayıcı**

### **2.3.2.4. Kuvvet algılama**

### **2.3.2.5. Moment (torque) algılama**

### **2.3.2.6. Uzaklık algılama (proximity sensor, yakın mesafe nesne algılama)**

#### **2.3.2.6.1. Optik uzaklık algılayıcı**

#### **2.3.2.6.2. Eddy akım algılayıcı**

#### **2.3.2.6.3. Ultrasonik yankı**

#### **2.3.2.6.4. Magnetik, Endüktif algılayıcılar**

#### **2.3.2.6.5. Kapasitif algılayıcılar.**

## **2.3.3. Temassız Dönüştürücüler**

## **2.4. Endüstriyel Uygulamalar**


# SENSORS OVERVIEW

- **Sensors:**  
Convert a Signal or Stimulus (Representing a Physical Property) into an Electrical Output
- **Transducers:**  
Convert One Type of Energy into Another
- **The Terms are often Interchanged**
- ***Active* Sensors Require an External Source of Excitation:**  
RTDs, Strain-Gages
- ***Passive* (Self-Generating) Sensors do not:**  
Thermocouples, Photodiodes


## TYPICAL SENSORS AND THEIR OUTPUTS

PROPERTY	SENSOR	ACTIVE/ PASSIVE	OUTPUT
Temperature	Thermocouple	Passive	Voltage
	Silicon	Active	Voltage/Current
	RTD	Active	Resistance
	Thermistor	Active	Resistance
Force / Pressure	Strain Gage	Active	Resistance
	Piezoelectric	Passive	Voltage
Acceleration	Accelerometer	Active	Capacitance
Position	LVDT	Active	AC Voltage
Light Intensity	Photodiode	Passive	Current

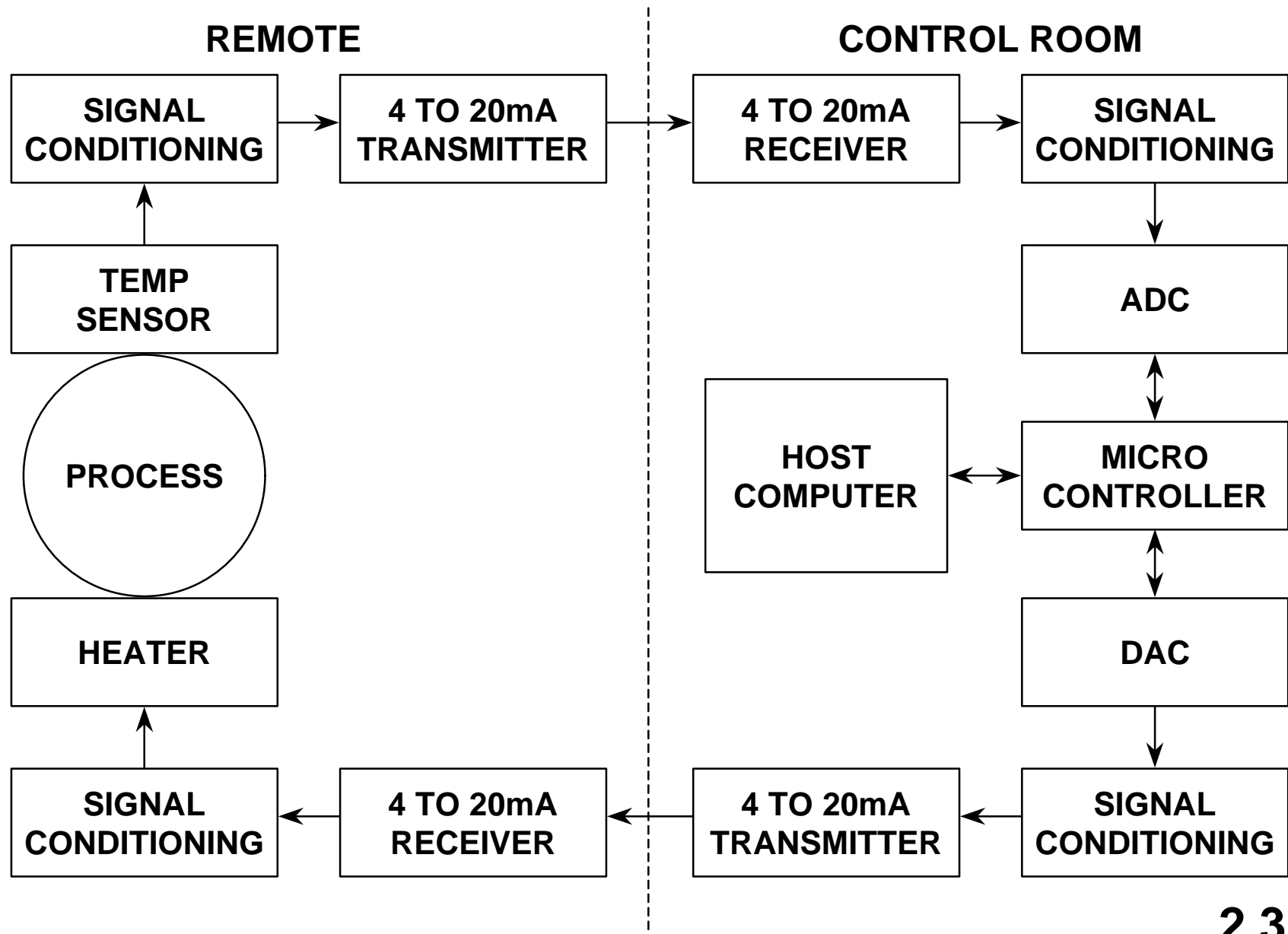
# TYPICAL INDUSTRIAL PROCESS CONTROL LOOP


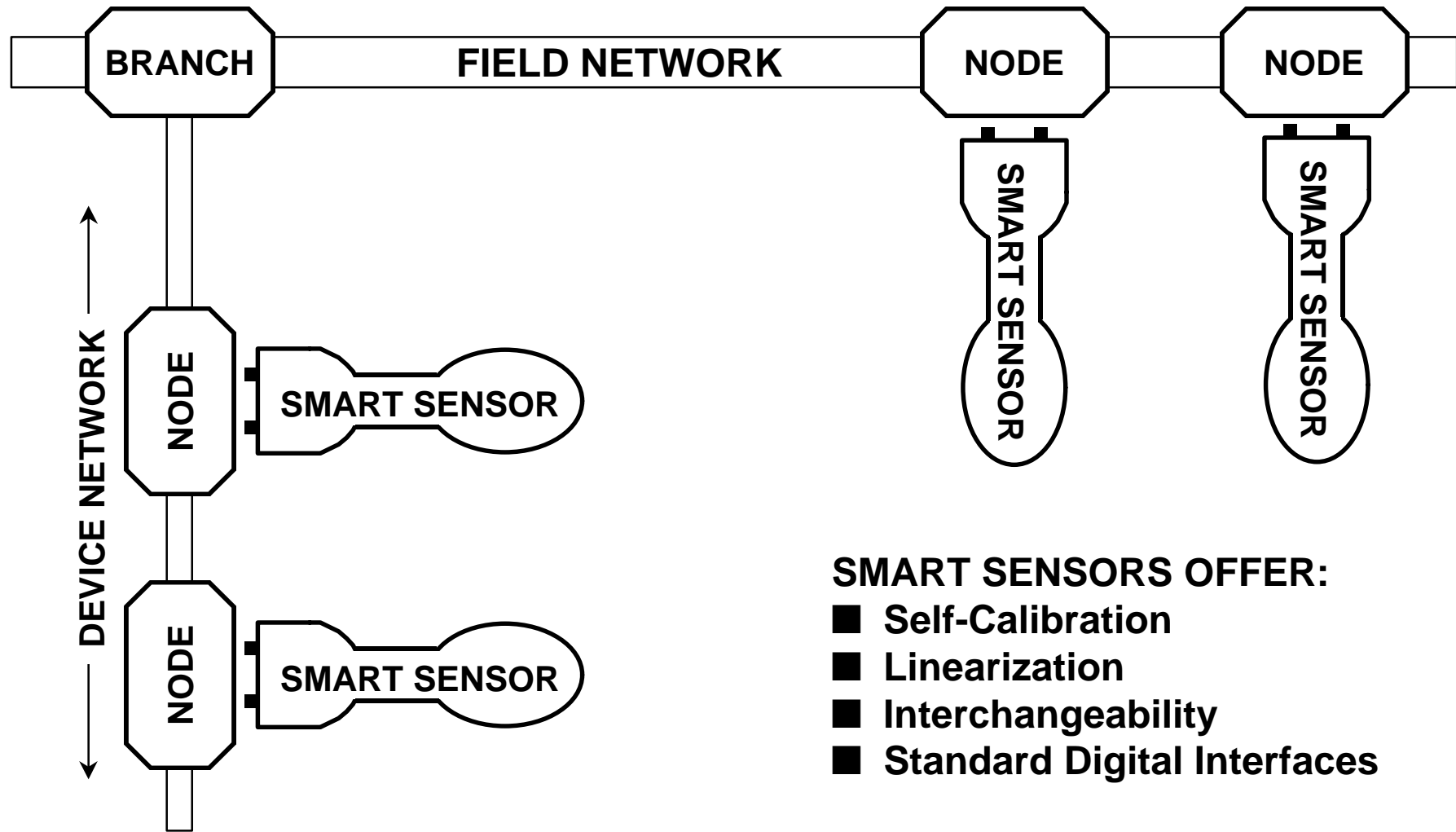
# STANDARDIZATION AT THE DIGITAL INTERFACE USING SMART SENSORS




# BASIC ELEMENTS IN A "SMART" SENSOR

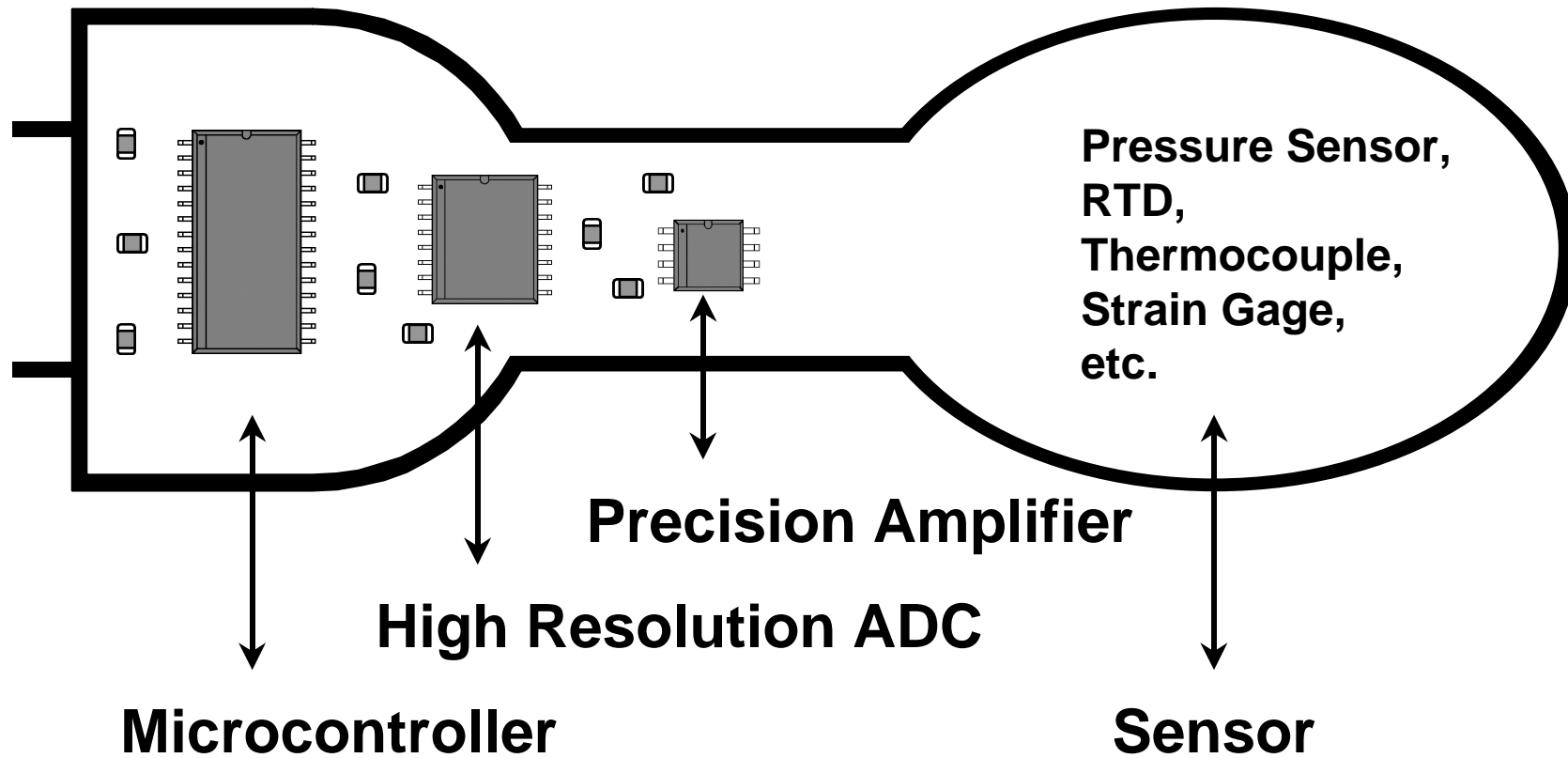


# RESISTANCE OF POPULAR SENSORS

■ Strain Gages	120Ω, 350Ω, 3500Ω
■ Weigh-Scale Load Cells	350Ω - 3500Ω
■ Pressure Sensors	350Ω - 3500Ω
■ Relative Humidity	100kΩ - 10MΩ
■ Resistance Temperature Devices (RTDs)	100Ω , 1000Ω
■ Thermistors	100Ω - 10MΩ
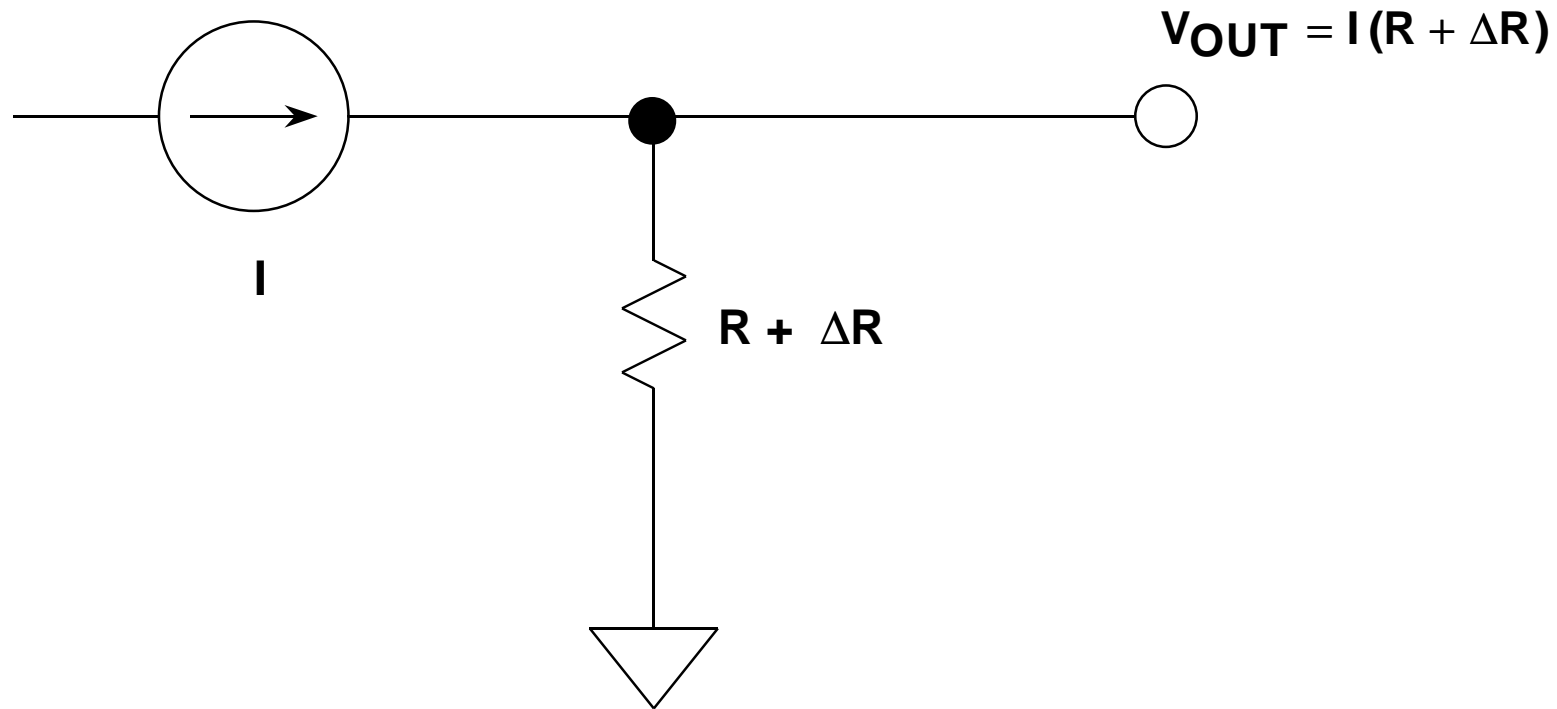
# MEASURING RESISTANCE INDIRECTLY USING A CONSTANT CURRENT SOURCE



# THE WHEATSTONE BRIDGE

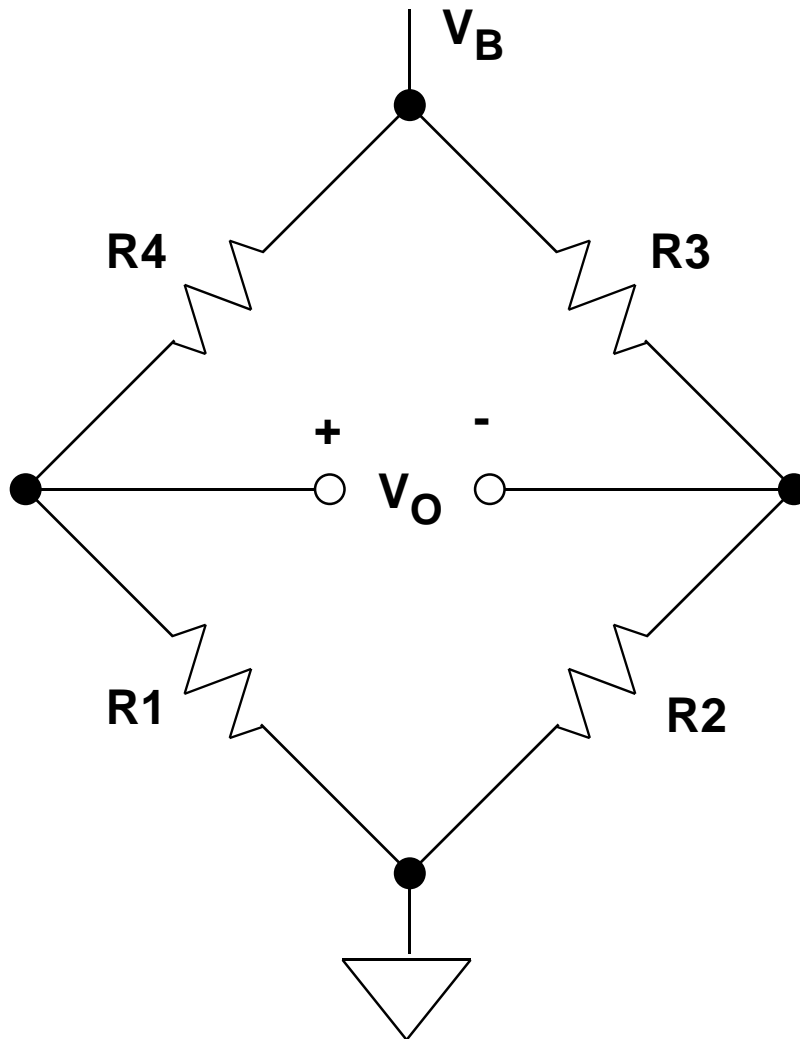


$$V_O = \frac{R_1}{R_1 + R_4} V_B - \frac{R_2}{R_2 + R_3} V_B$$
$$= \frac{\frac{R_1}{R_4} - \frac{R_2}{R_3}}{\left(1 + \frac{R_1}{R_4}\right) \left(1 + \frac{R_2}{R_3}\right)} V_B$$

AT BALANCE,

$$V_O = 0 \quad \text{IF} \quad \frac{R_1}{R_4} = \frac{R_2}{R_3}$$
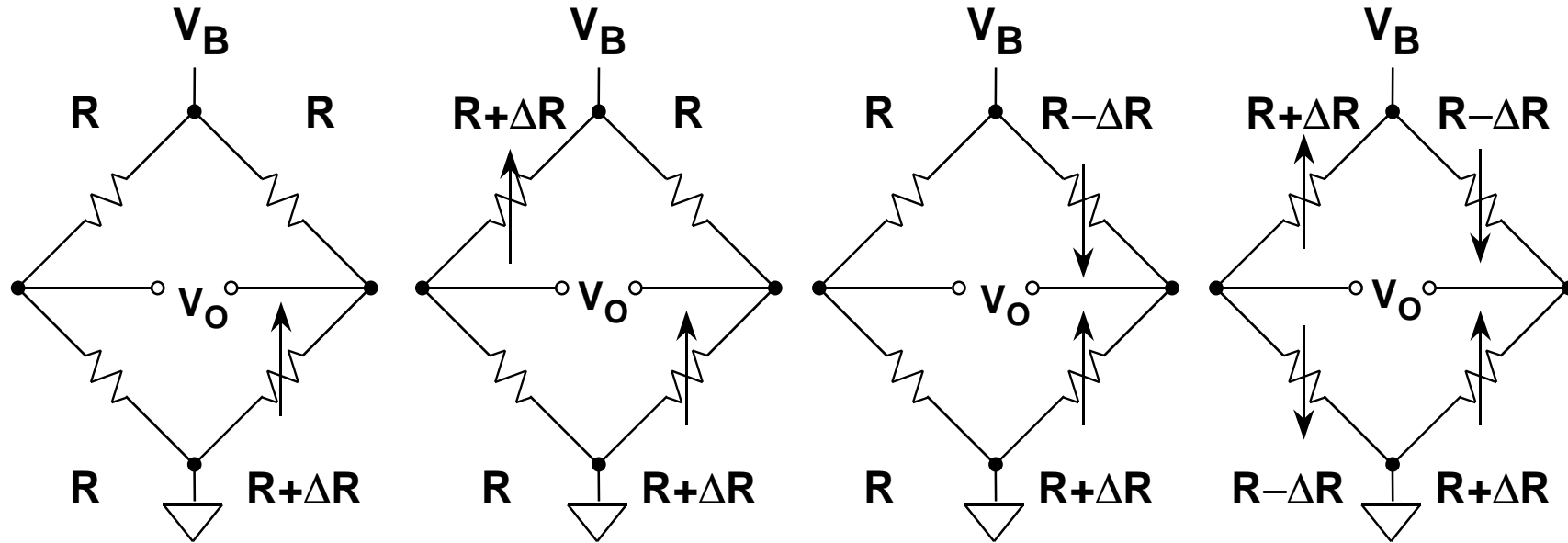
# OUTPUT VOLTAGE AND LINEARITY ERROR FOR CONSTANT VOLTAGE DRIVE BRIDGE CONFIGURATIONS



$V_O:$	$\frac{V_B}{4} \left[ \frac{\Delta R}{R + \frac{\Delta R}{2}} \right]$	$\frac{V_B}{2} \left[ \frac{\Delta R}{R + \frac{\Delta R}{2}} \right]$	$\frac{V_B}{2} \left[ \frac{\Delta R}{R} \right]$	$V_B \left[ \frac{\Delta R}{R} \right]$
--------	--	--	---	---

<b>Linearity Error:</b>	0.5%/%	0.5%/%	0	0
-------------------------	--------	--------	---	---


**(A) Single-Element Varying**

**(B) Two-Element Varying (1)**

**(C) Two-Element Varying (2)**

**(D) All-Element Varying**
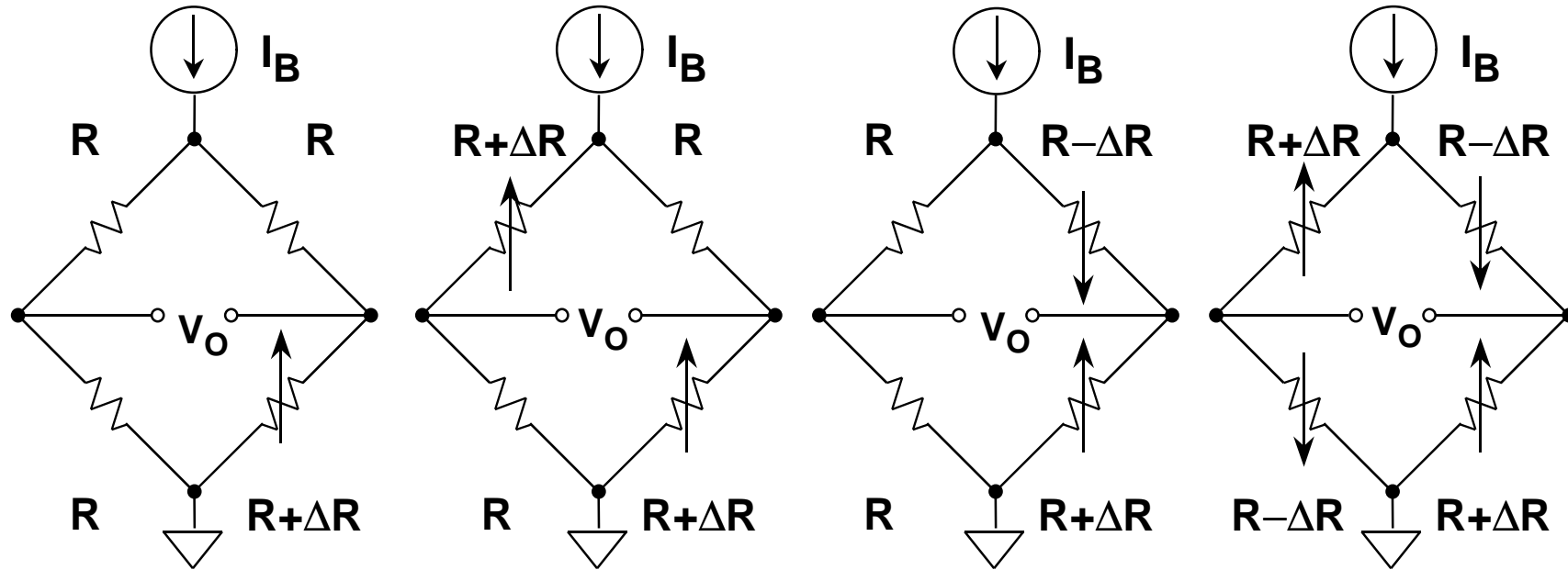
# OUTPUT VOLTAGE AND LINEARITY ERROR FOR CONSTANT CURRENT DRIVE BRIDGE CONFIGURATIONS



---

$V_O:$	$\frac{I_B R}{4} \left[ \frac{\Delta R}{R + \frac{\Delta R}{4}} \right]$	$\frac{I_B}{2} \left[ \Delta R \right]$	$\frac{I_B}{2} \left[ \Delta R \right]$	$I_B \left[ \Delta R \right]$
--------	--	---	---	-------------------------------

---

<b>Linearity Error:</b>	<b>0.25%/%</b>	<b>0</b>	<b>0</b>	<b>0</b>
-------------------------	----------------	----------	----------	----------

---

**(A) Single-Element Varying**

**(B) Two-Element Varying (1)**


**(C) Two-Element Varying (2)**

**(D) All-Element Varying**

# BRIDGE CONSIDERATIONS

- **Selecting Configuration (1, 2, 4 - Element Varying)**
- **Selection of Voltage or Current Excitation**
- **Stability of Excitation Voltage or Current**
- **Bridge Sensitivity: FS Output / Excitation Voltage**  
**1mV / V to 10mV / V Typical**
- **Fullscale Bridge Outputs: 10mV - 100mV Typical**
- **Precision, Low Noise Amplification / Conditioning**  
**Techniques Required**
- **Linearization Techniques May Be Required**
- **Remote Sensors Present Challenges**

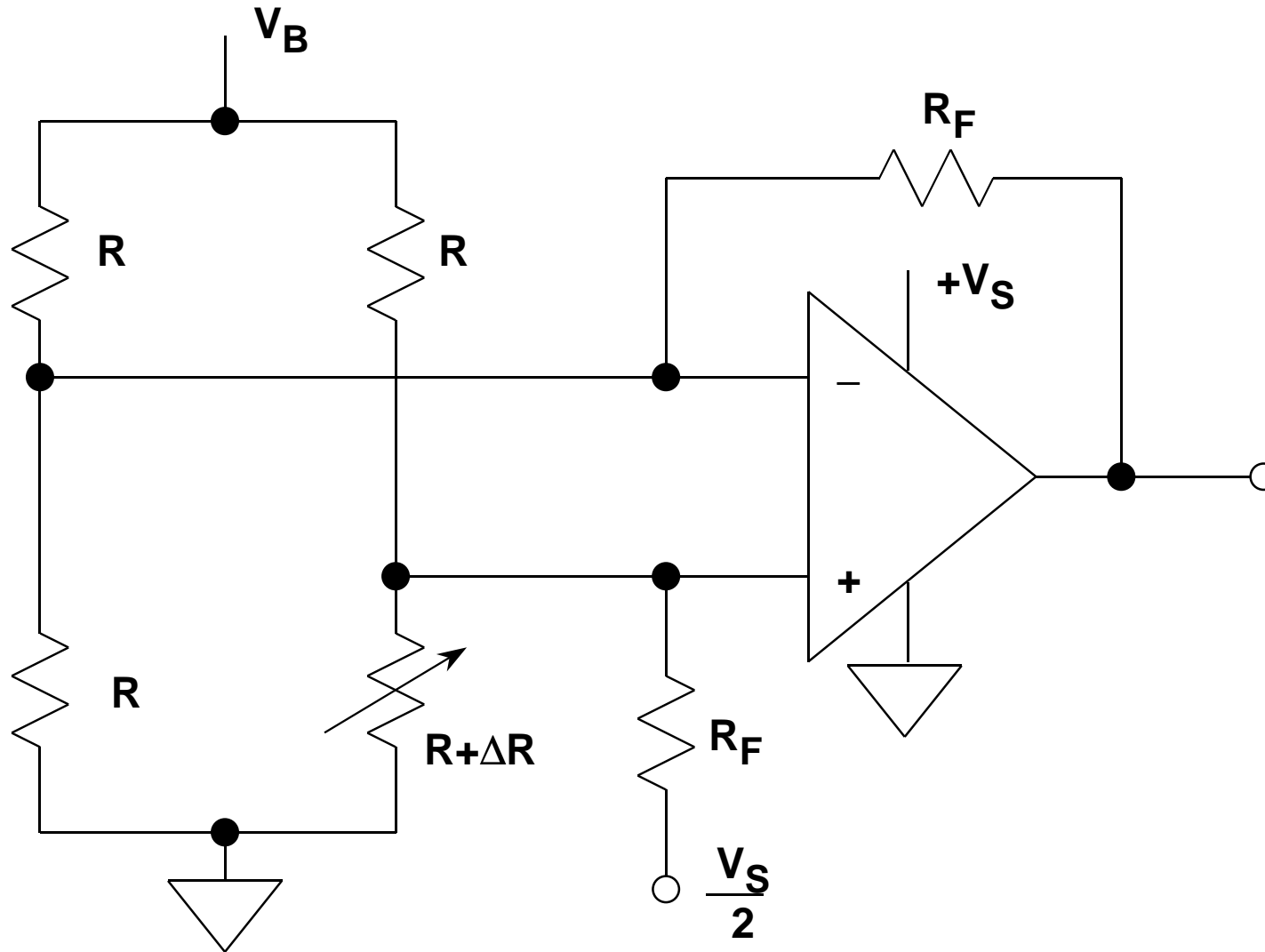
# USING A SINGLE OP AMP AS A BRIDGE AMPLIFIER FOR A SINGLE-ELEMENT VARYING BRIDGE




a

2.7
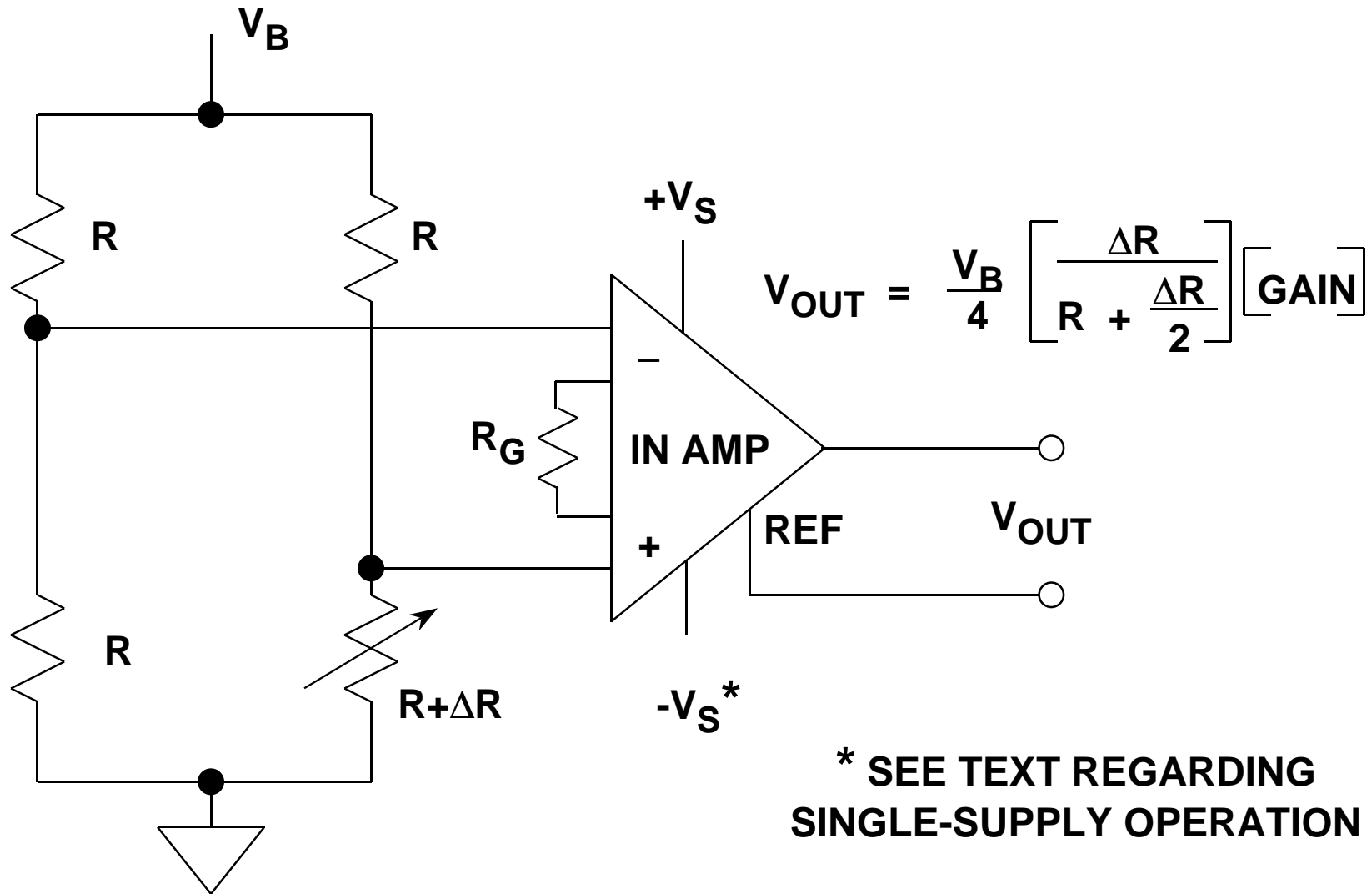
# USING AN INSTRUMENTATION AMPLIFIER WITH A SINGLE-ELEMENT VARYING BRIDGE



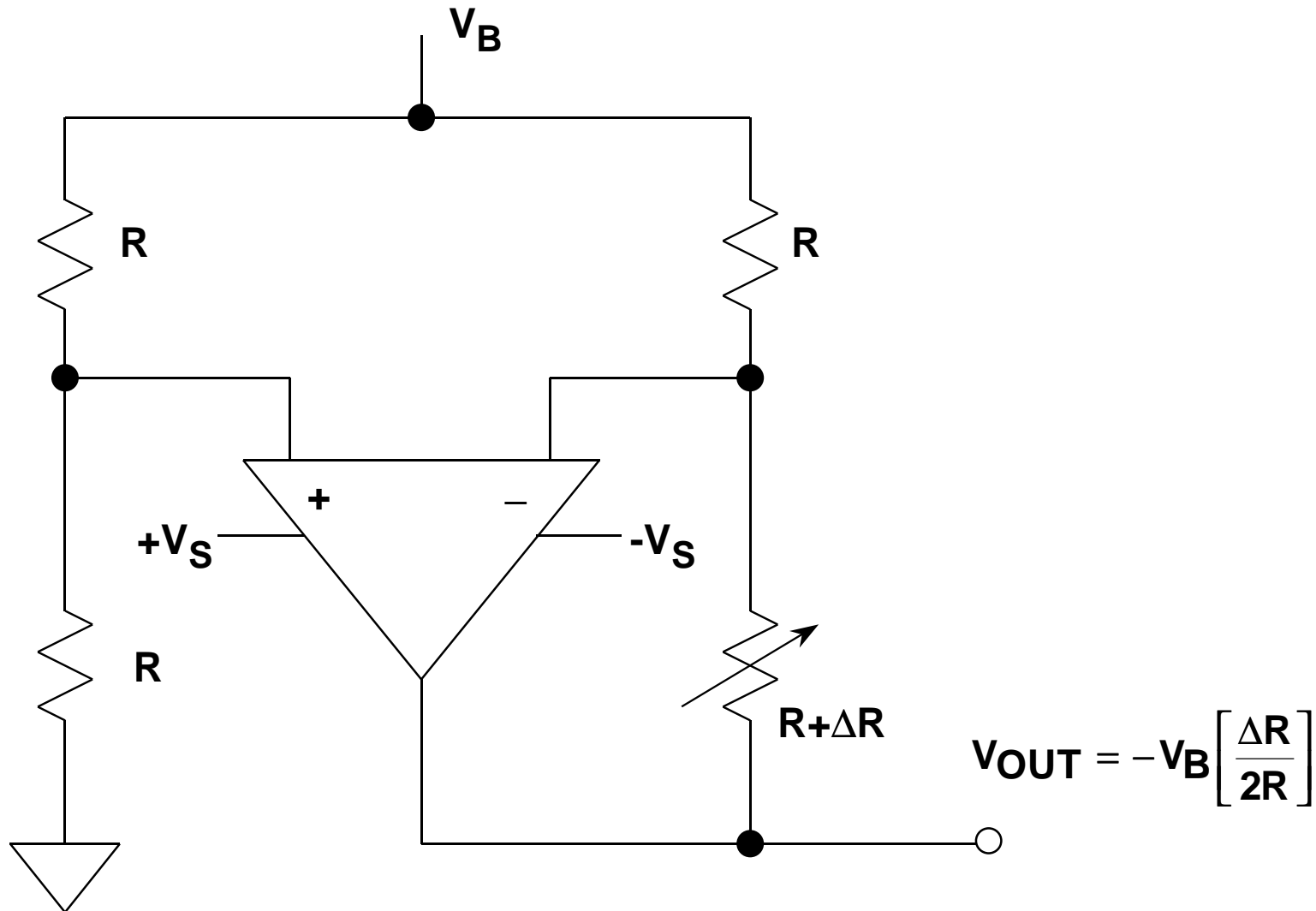
# LINEARIZING A SINGLE-ELEMENT VARYING BRIDGE METHOD 1



a

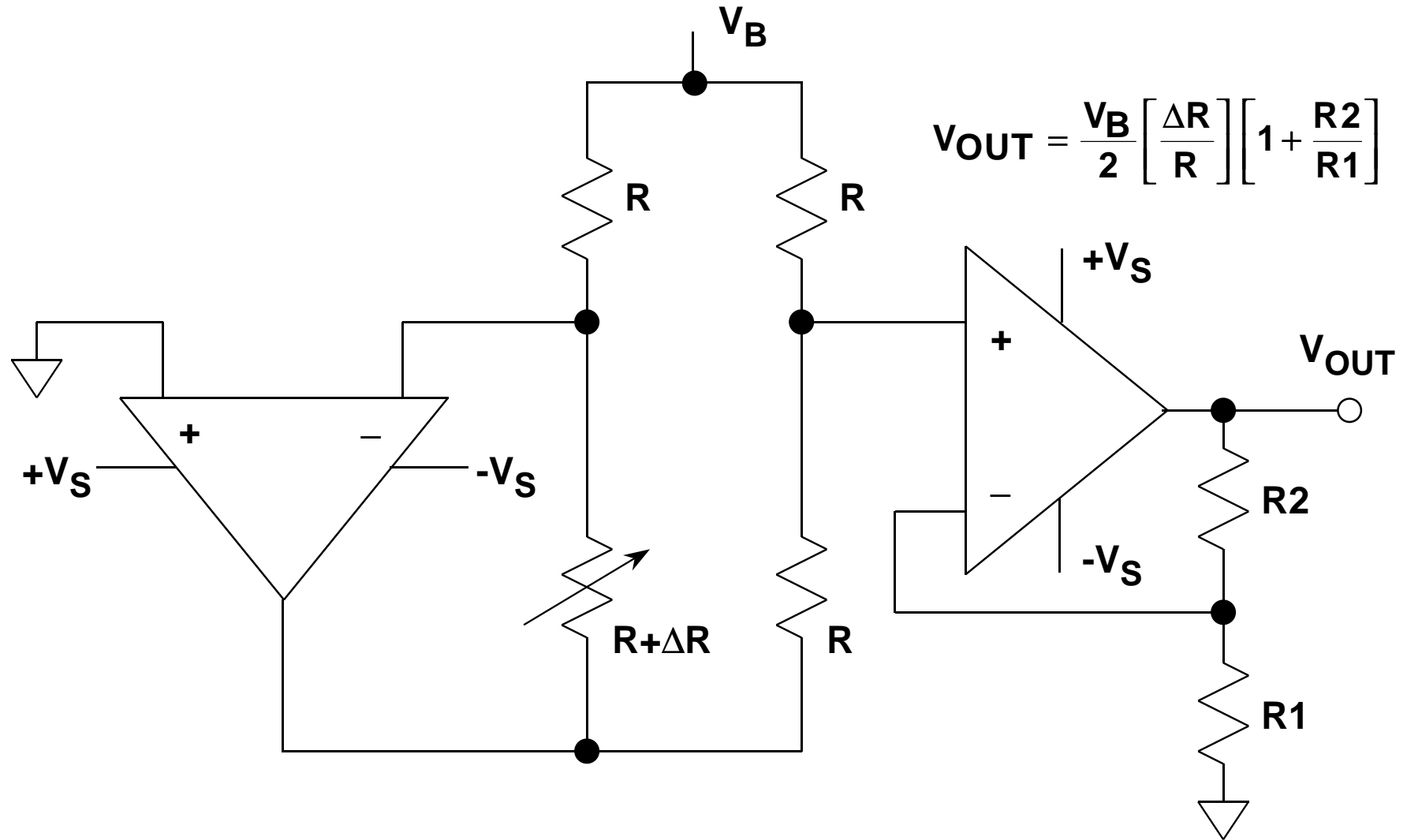
# LINEARIZING A SINGLE-ELEMENT VARYING BRIDGE METHOD 2



a


2.10
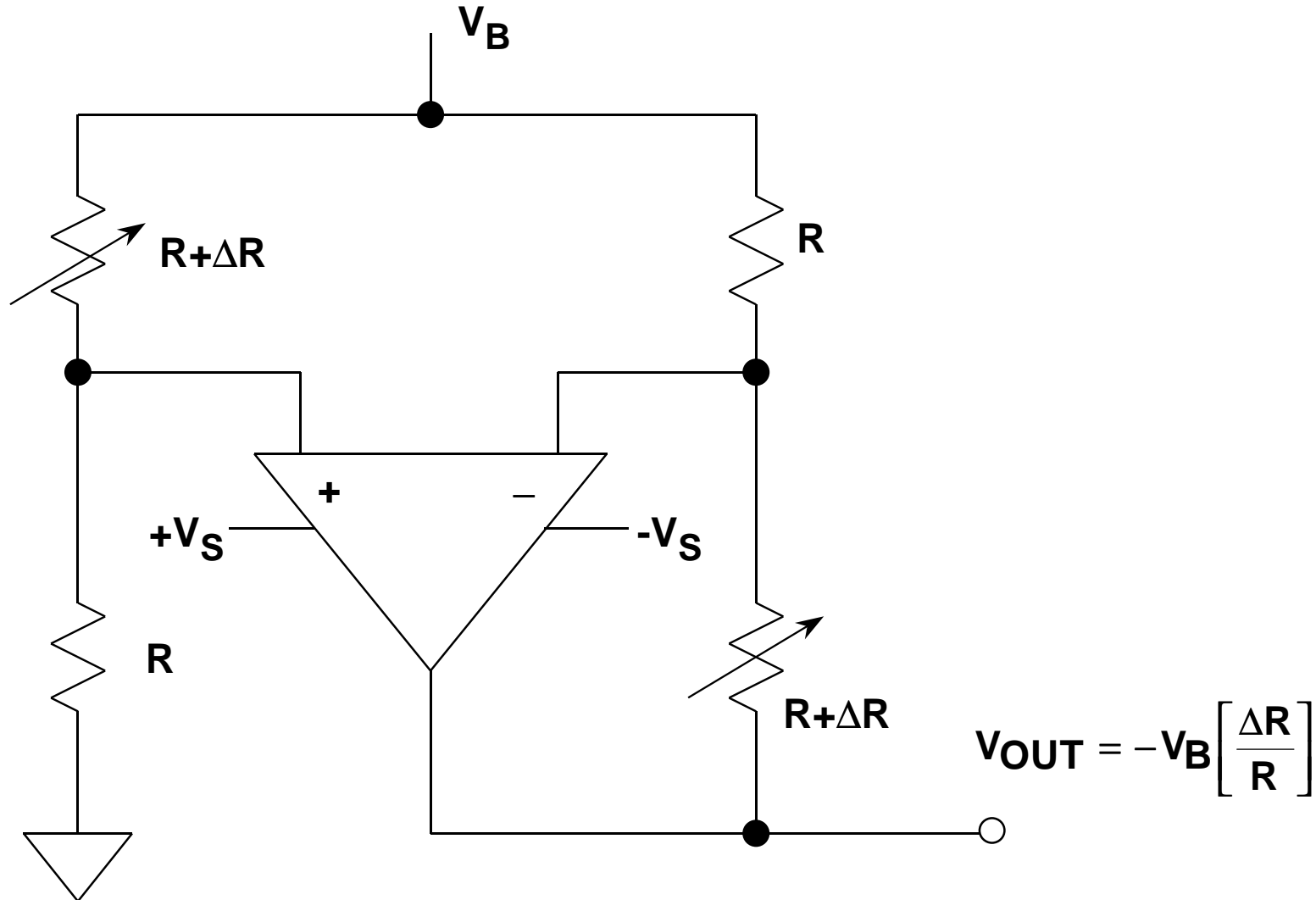
# LINEARIZING A TWO-ELEMENT VARYING BRIDGE METHOD 1 (CONSTANT VOLTAGE DRIVE)




a
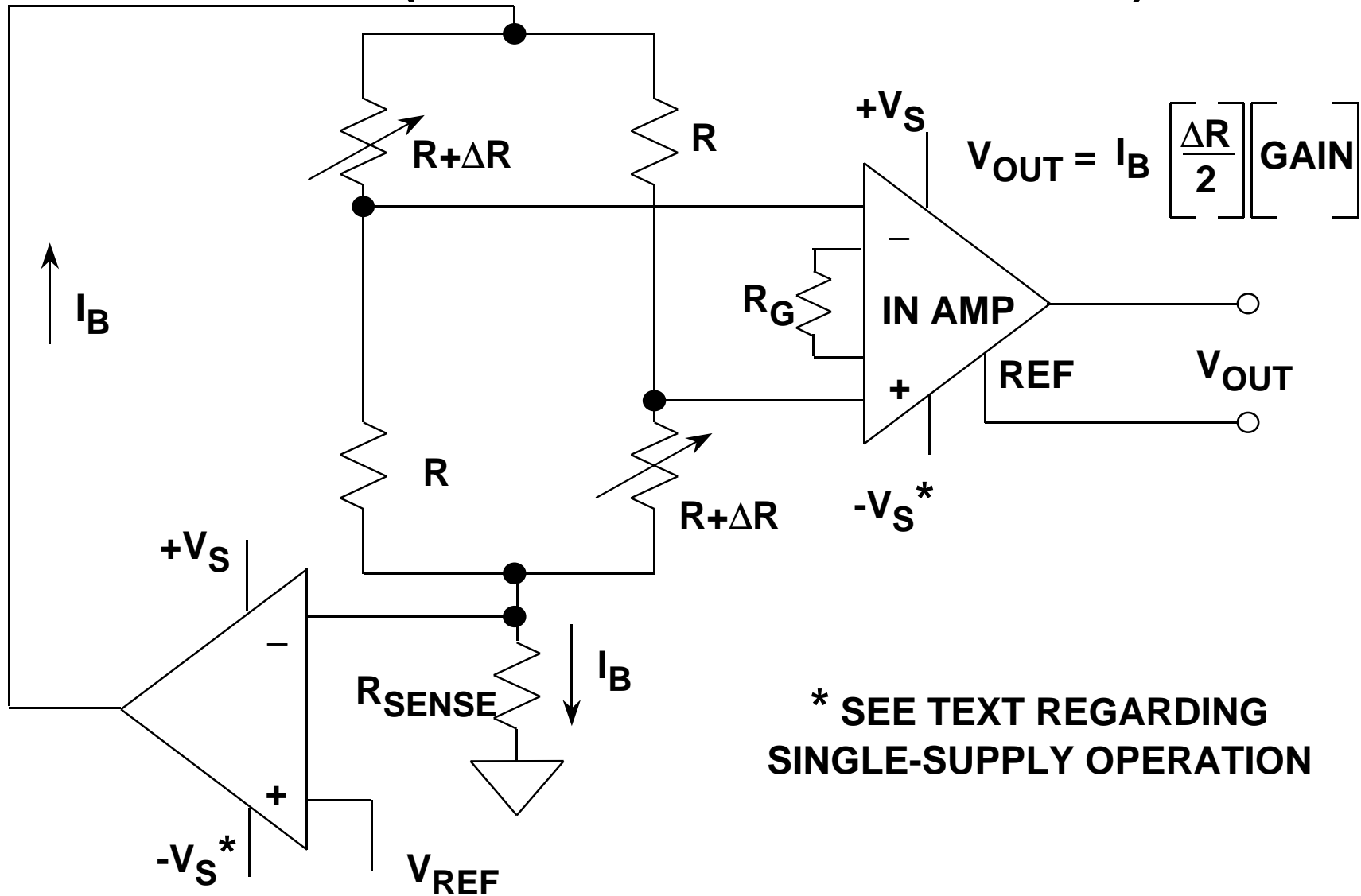
# LINEARIZING A TWO-ELEMENT VARYING BRIDGE METHOD 2 (CONSTANT CURRENT DRIVE)



\* SEE TEXT REGARDING  
SINGLE-SUPPLY OPERATION

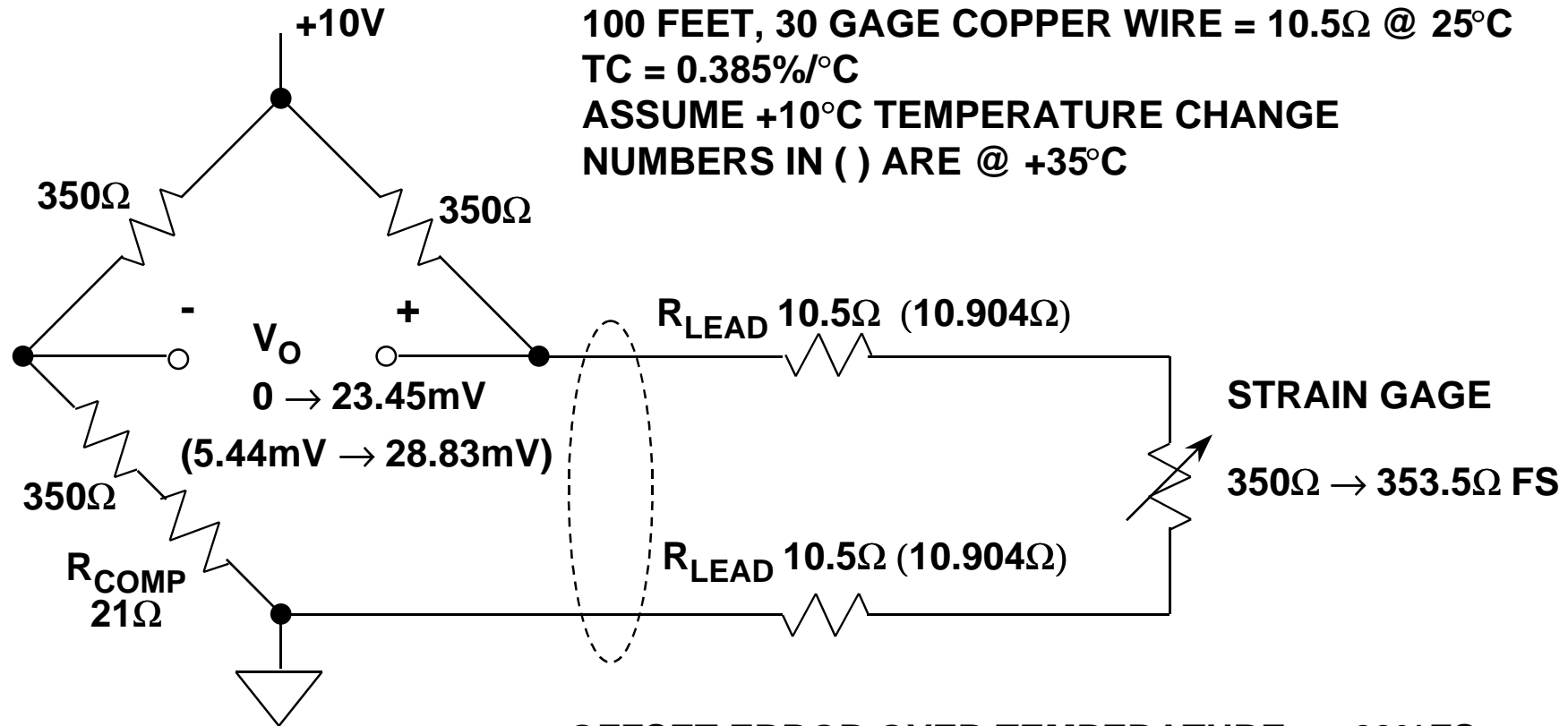
# ERRORS PRODUCED BY WIRING RESISTANCE FOR REMOTE RESISTIVE BRIDGE SENSOR



100 FEET, 30 GAGE COPPER WIRE =  $10.5\Omega @ 25^\circ C$   
 $TC = 0.385\%/^\circ C$   
 ASSUME  $+10^\circ C$  TEMPERATURE CHANGE  
 NUMBERS IN ( ) ARE @  $+35^\circ C$

**OFFSET ERROR OVER TEMPERATURE =  $+23\%FS$**   
**GAIN ERROR OVER TEMPERATURE =  $-0.26\%FS$**
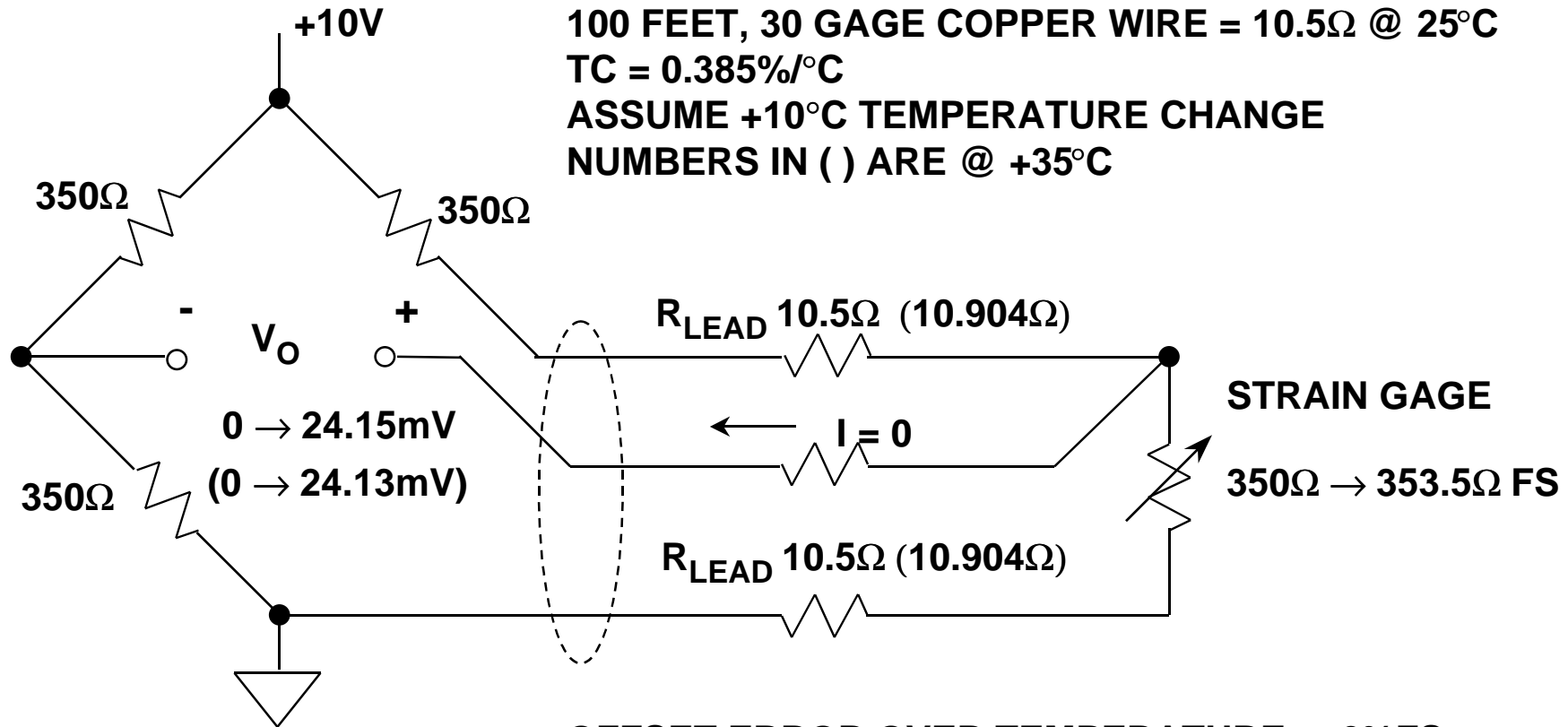
# 3-WIRE CONNECTION TO REMOTE BRIDGE ELEMENT (SINGLE-ELEMENT VARYING)




100 FEET, 30 GAGE COPPER WIRE =  $10.5\Omega @ 25^\circ C$   
 TC =  $0.385\%/^\circ C$   
 ASSUME  $+10^\circ C$  TEMPERATURE CHANGE  
 NUMBERS IN ( ) ARE @  $+35^\circ C$

OFFSET ERROR OVER TEMPERATURE =  $0\%FS$


GAIN ERROR OVER TEMPERATURE =  $-0.08\%FS$
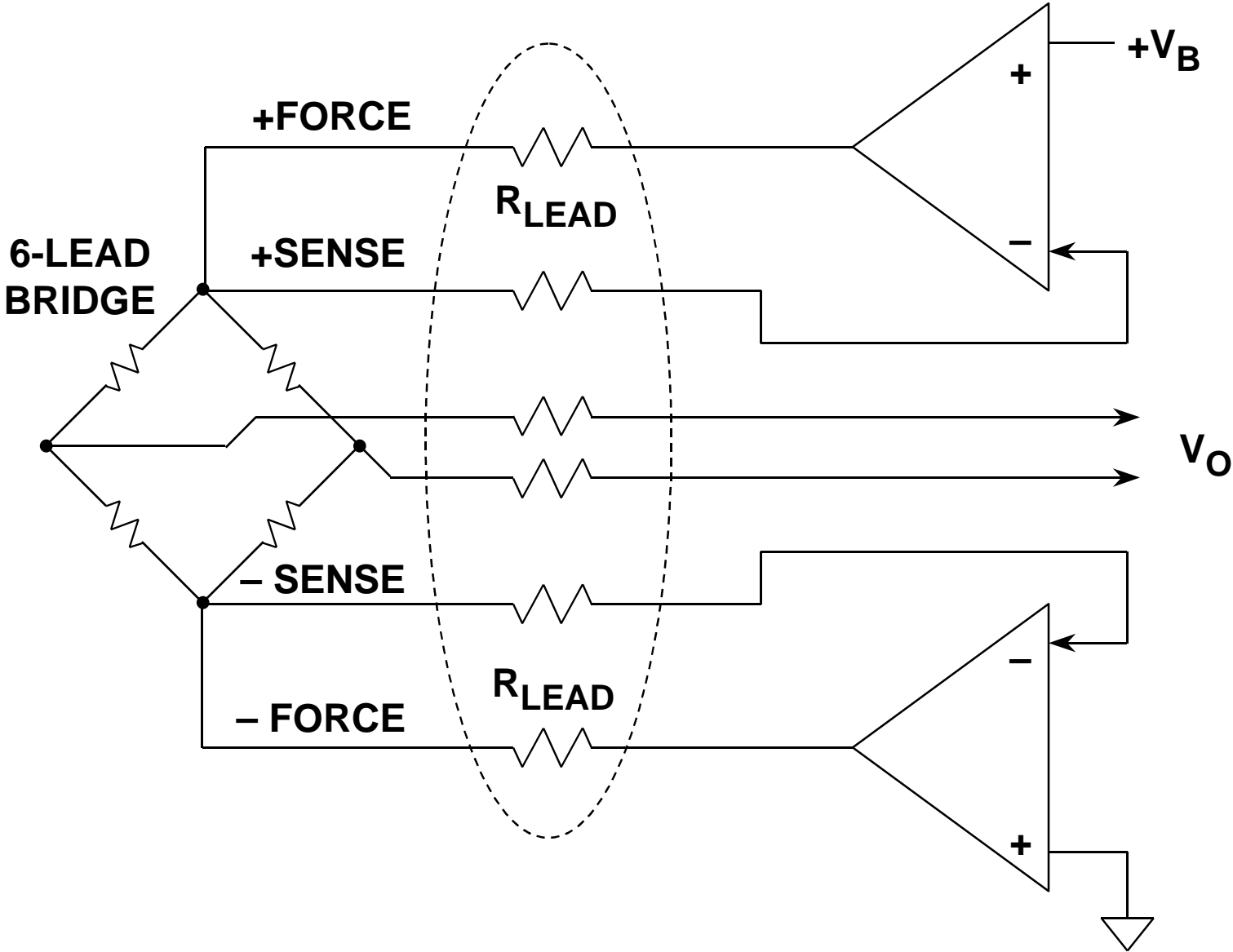
# KELVIN (4-WIRE) SENSING MINIMIZES ERRORS DUE TO LEAD RESISTANCE




a
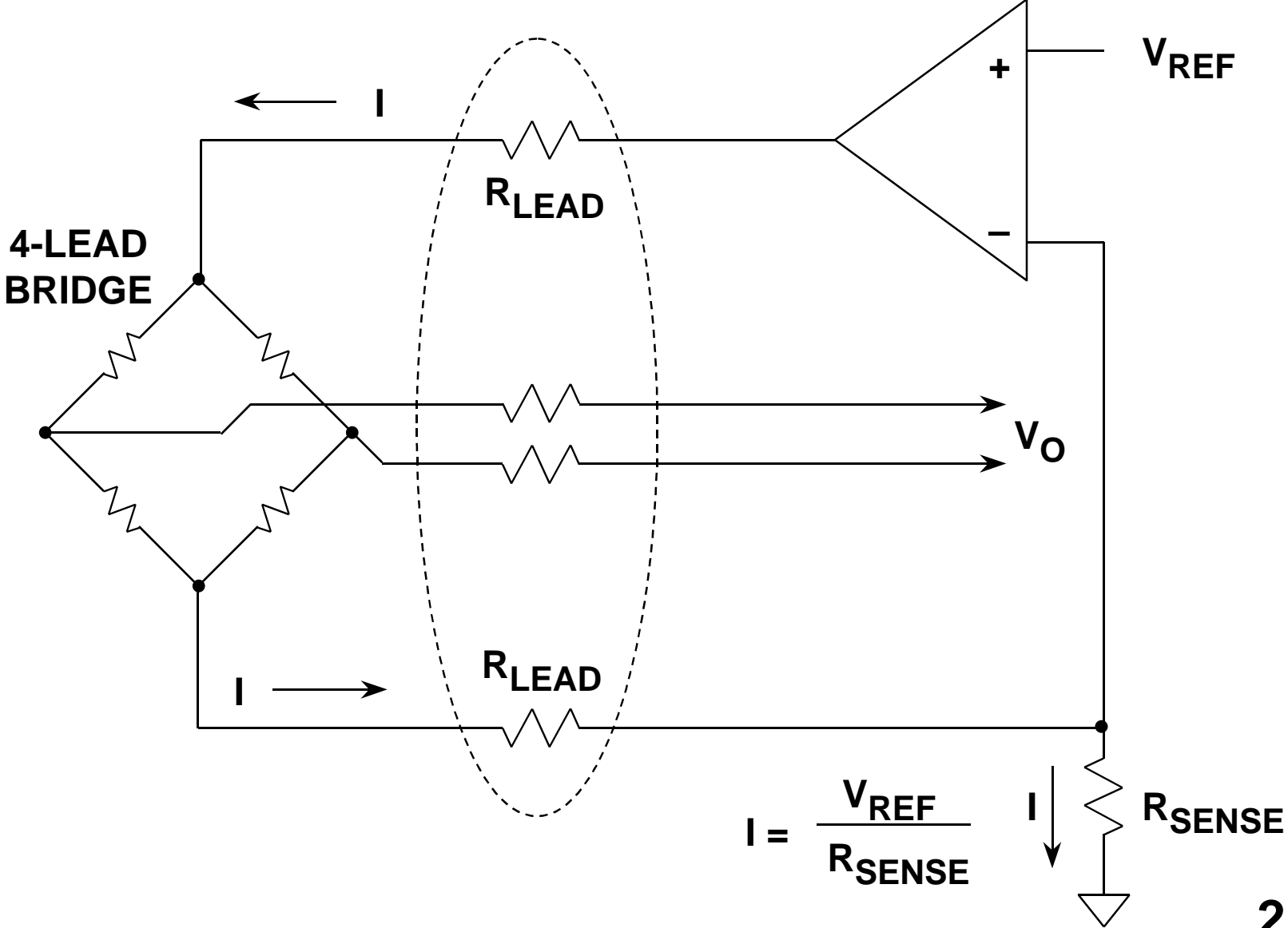
# CONSTANT CURRENT EXCITATION MINIMIZES WIRING RESISTANCE ERRORS



a

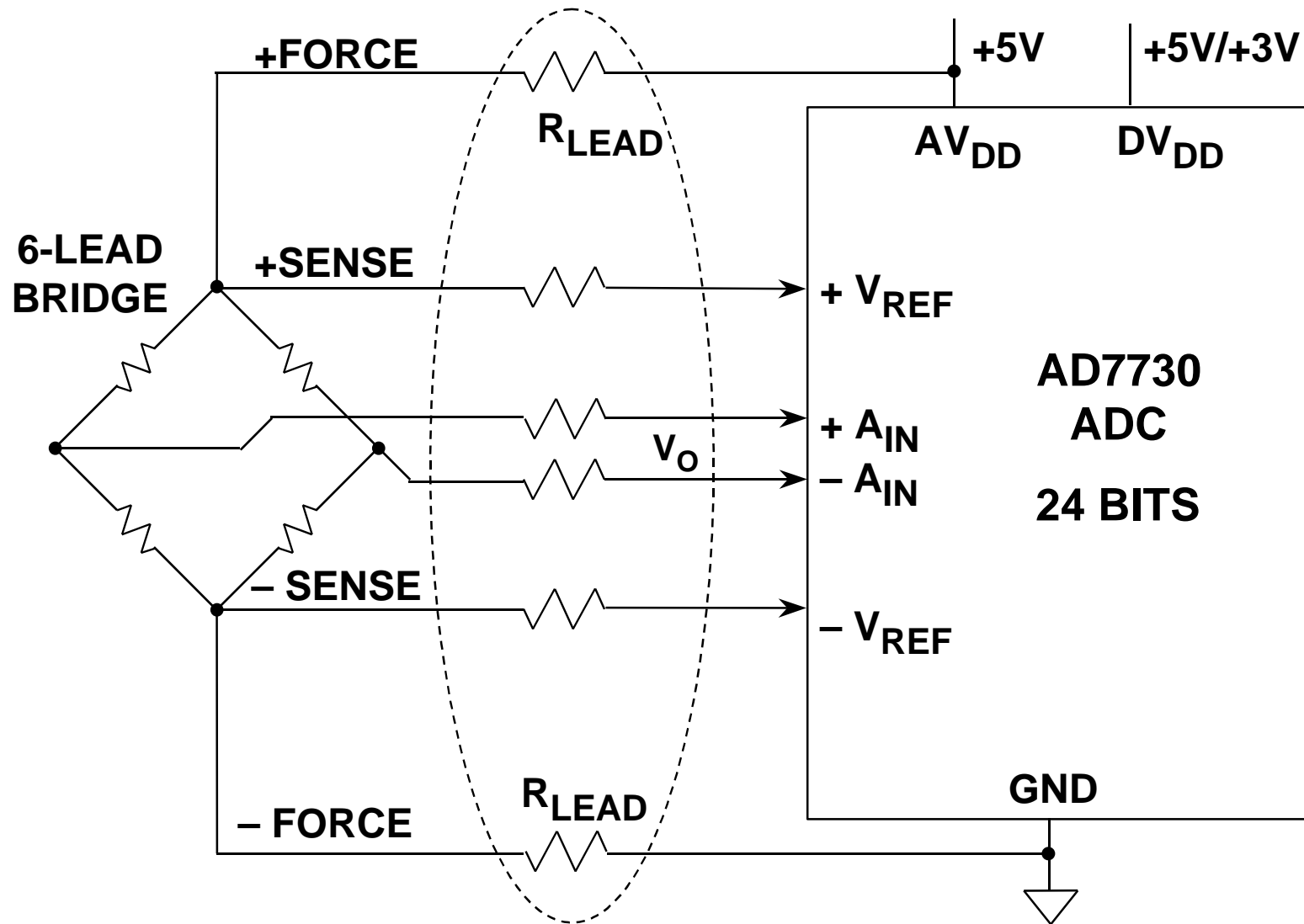
# DRIVING REMOTE BRIDGE USING KELVIN (4-WIRE) SENSING AND RATIOMETRIC CONNECTION TO ADC




a

2.17


# TYPICAL SOURCES OF OFFSET VOLTAGE

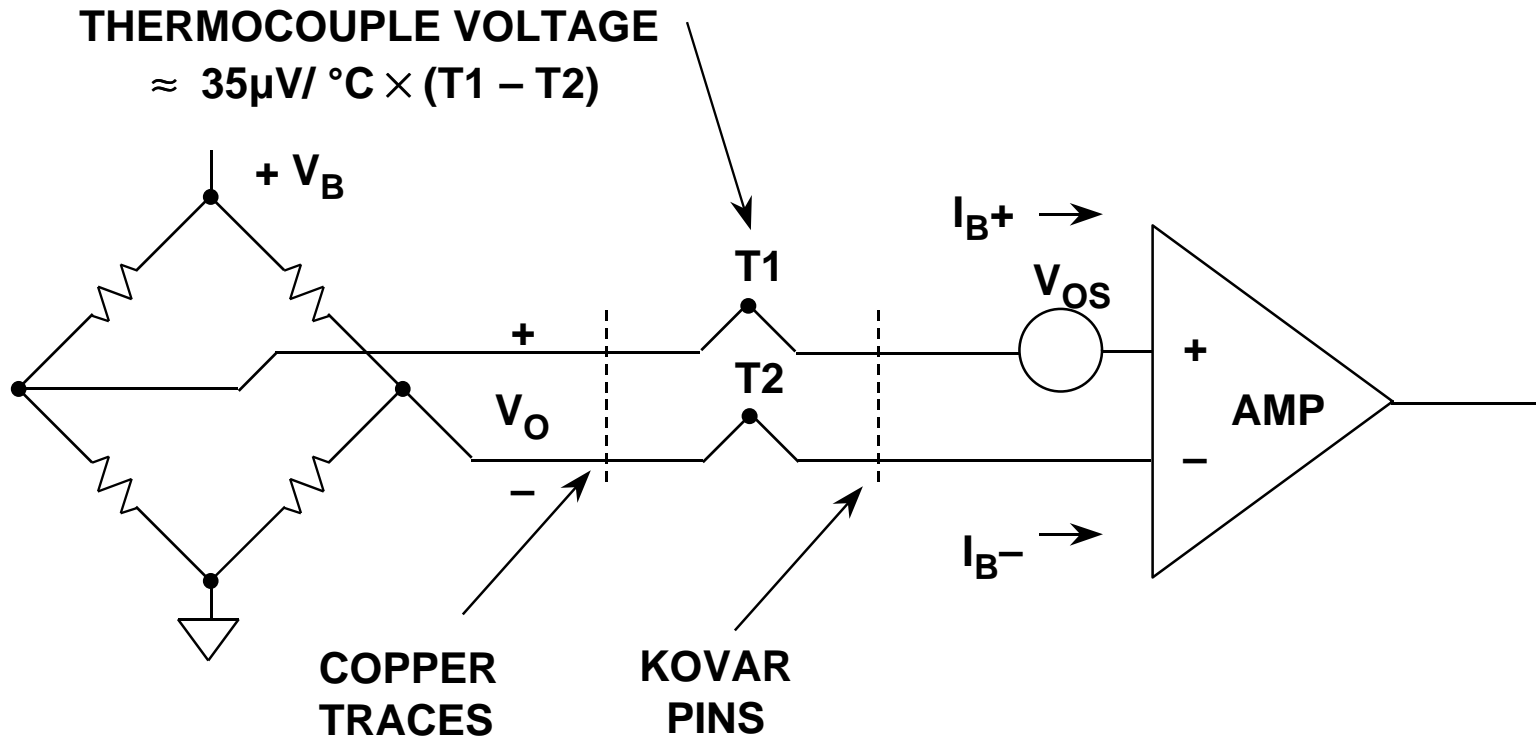

# AC EXCITATION MINIMIZES OFFSET ERRORS

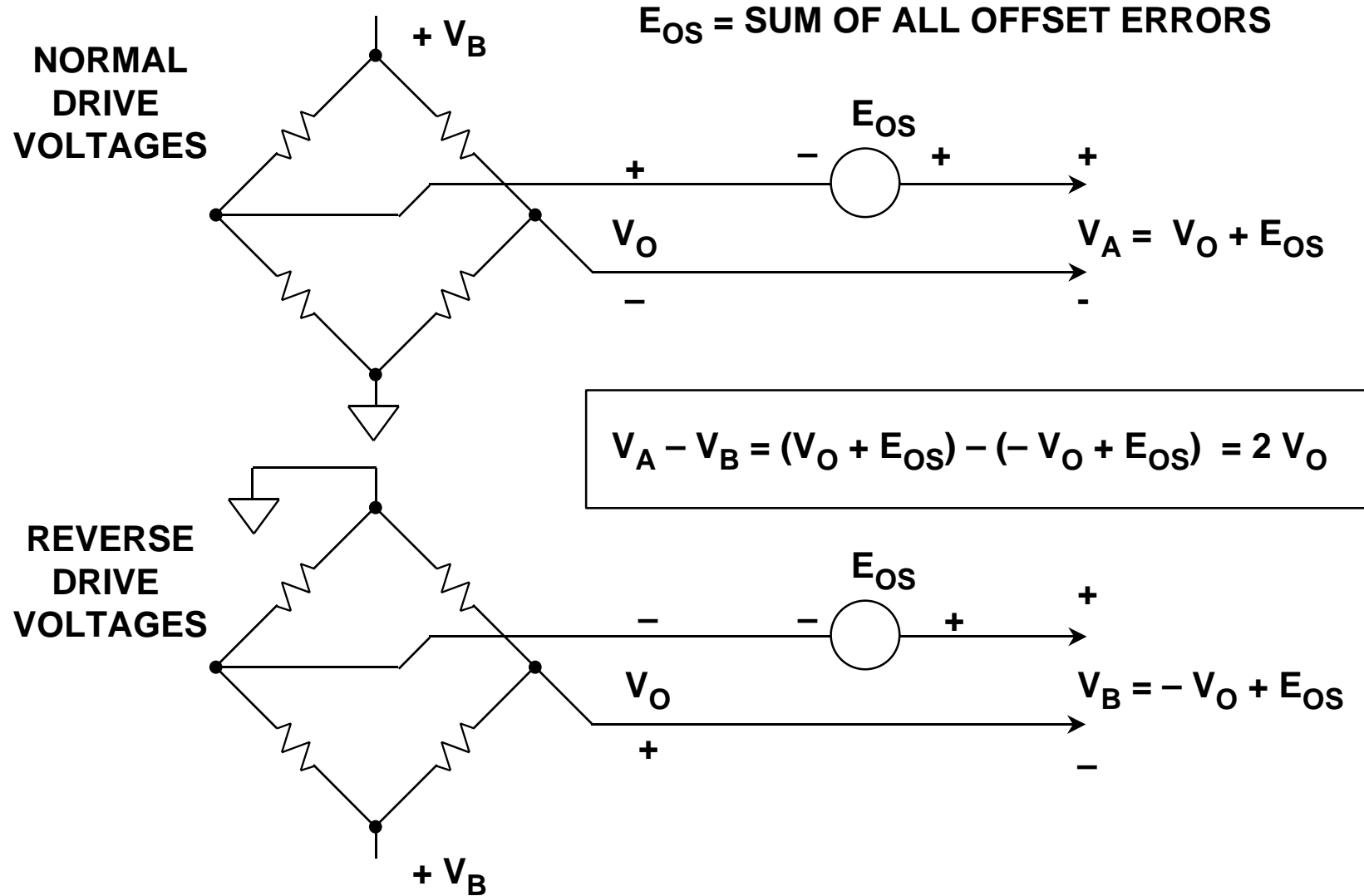

# SIMPLIFIED AC BRIDGE DRIVE CIRCUIT

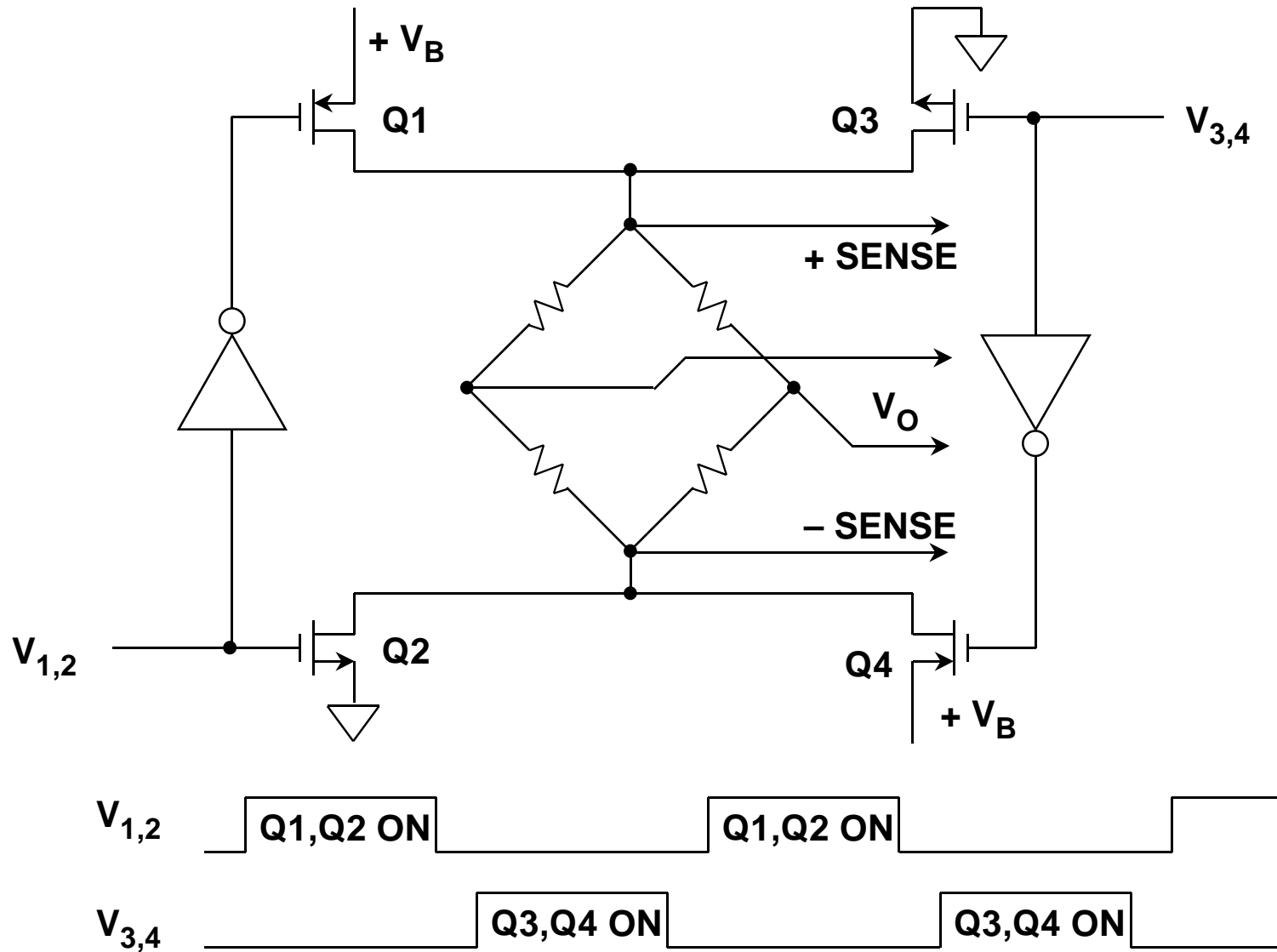

a